

ECE271, Final Project

Ben Adams, Grant Haines, Benjiman Walsh

December 1, 2019

Contents

1	Introduction	2
2	High Level Descriptions	2
3	Controller Descriptions	2
3.1	NES Controller	2
4	HDL Components	3
5	Appendix	3
5.1	Source Code	3
5.1.1	NES Controller Reader	3
5.1.2	Square Wave Generator	3
5.2	Simulation Results	4
5.2.1	NES Controller Reader	4
5.2.2	Square Wave Generator	5

1 Introduction

The purpose of this project is to create a digital logic design that uses various input modules with various output modules.

2 High Level Descriptions

3 Controller Descriptions

This section is meant to provide a brief but thorough low-level view of the operations of our chosen input devices.

3.1 NES Controller

The Nintendo Entertainment System (NES) first became available in America in 1985 and revolutionized society as the first accessible home video game system. NES controllers work by receiving "clock" and "latch" signals from the NES console and transmitting a data signal to the console. NES controllers use a shift register to store all of the controller's button data when the console sends the latch signal (As in figure 1). Each successive clock signal shifts the controller register down and the controller's data wire outputs a value that represents the next button's signal (See figure 2).

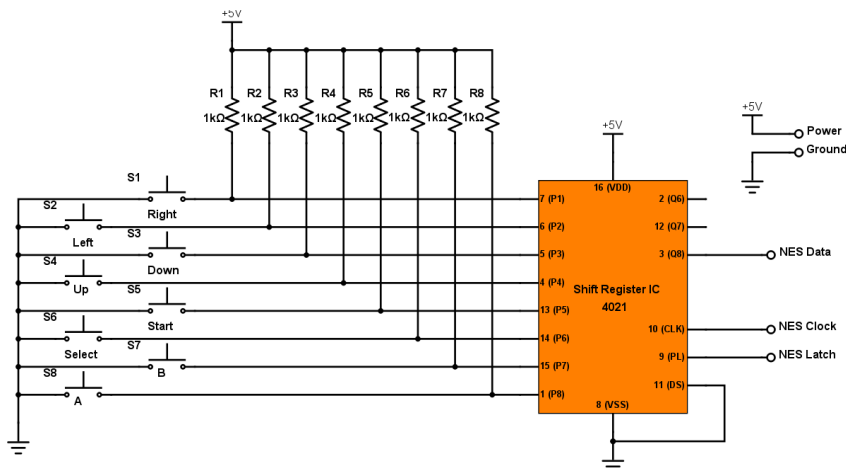


Figure 1: "Button Mashing" on the NES

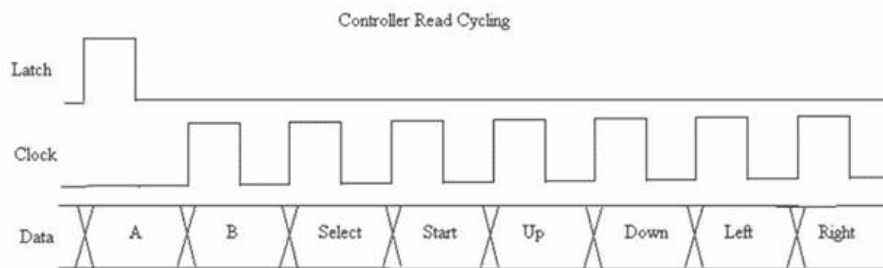


Figure 2: "Button Mashing" on the NES

The NES controller decoder SystemVerilog module was provided for us in the course materials.

4 HDL Components

5 Appendix

5.1 Source Code

5.1.1 NES Controller Reader

5.1.2 Square Wave Generator

```
module periodTime(input logic clk,
                  input logic [2:0] data,
                  output logic q);

int compareNumber;
int count;

always_comb
    case(data)
        0: compareNumber = 6400; // just mod input clock until audio spectrum periods
        1: compareNumber = 3200; // one octave
        2: compareNumber = 1600;
        3: compareNumber = 8000;
```

```

        4: compareNumber = 4000;
        5: compareNumber = 2000;
        6: compareNumber = 1000;
        7: compareNumber = 500;           // consider adding default case
    endcase

always_ff @(posedge clk)
    begin
        if (count >= compareNumber)      // could modify to not restart notes when changed
            count <= 0;
        else
            count <= count + 1;
        end

always_comb
    begin
        if( count < compareNumber)
            q = (count > compareNumber/2);    //assigns output with initial low
        else
            q = 0;
        end
    end

endmodule

```

5.2 Simulation Results

5.2.1 NES Controller Reader

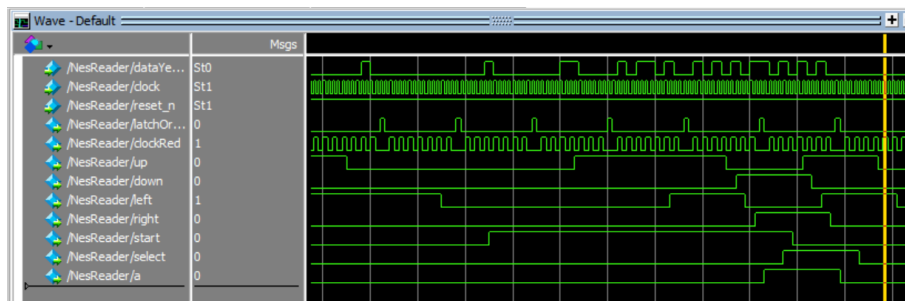


Figure 3: "Button Mashing" on the NES

At first, I wanted to test the NES controller reader by just simulating a bunch of random inputs as seen in Figure 3. I remembered the NES game CONTRA had a cheat code that involved most of the controller's buttons (all but SELECT). The "Contra Code" was then simulated I'm gonna rewrite this.



Figure 4: CONTRA screenshot

 


Figure 5: Simulating the "Contra Code"

```

force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    1 {80 ps} , 0 {100 ps} , 0 {120 ps} , 0 {140 ps} #up
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 1 {100 ps} , 0 {120 ps} , 0 {140 ps} #down
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    1 {80 ps} , 0 {100 ps} , 0 {120 ps} , 0 {140 ps} #up
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 1 {100 ps} , 0 {120 ps} , 0 {140 ps} #down
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 1 {120 ps} , 0 {140 ps} #left
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 0 {120 ps} , 1 {140 ps} #right
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 1 {120 ps} , 0 {140 ps} #left
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 0 {120 ps} , 1 {140 ps} #right
force -freeze sim:/NesReader/dataYellow 0 0, 1 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 0 {120 ps} , 0 {140 ps} #b
force -freeze sim:/NesReader/dataYellow 1 0, 0 {20 ps} , 0 {40 ps} , 0 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 0 {120 ps} , 0 {140 ps} #a
force -freeze sim:/NesReader/dataYellow 0 0, 0 {20 ps} , 0 {40 ps} , 1 {60 ps} ,
    0 {80 ps} , 0 {100 ps} , 0 {120 ps} , 0 {140 ps} start

```

5.2.2 Square Wave Generator

 


Figure 6: Simulating button inputs to control the square wave oscillator